

Design Idea DI-61

TinySwitch-II[®] 3 W Charger: <200 mW No-load Consumption



Application	Device	Power Output	Input Voltage	Output Voltage	Topology
Charger	TNY264P	3 W	85-265 VAC	5 V, 600 mA	Flyback

Design Highlights

- Less than 200 mW no-load power consumption (for 115 or 230 VAC input)
- Meets CISPR-22 Class B without Y capacitor
- Low cost, low component count solution

Operation

The *TinySwitch-II* flyback converter in Figure 1 generates a constant voltage, constant current (CV/CC) 5 V, 600 mA output. Typical applications include wall-mounted chargers for cell phones, PDAs and other battery powered portable equipment.

The key performance characteristic of the circuit shown is the extremely low no-load consumption of <200 mW. A linear transformer charger of similar rating will typically consume 1 W to 4 W at no-load. At \$0.12/kWh, the *TinySwitch-II* can therefore reduce energy costs by \$1 to \$4 per year.

The no-load performance is achieved by use of *TinySwitch-II*, and by careful transformer design.

The circuit meets CISPR-22 Class B conducted EMI limits without a Y capacitor, and therefore has very low AC leakage current. This EMI performance is achieved via the *TinySwitch-II* internal jitter, use of a shield winding, an output RC snubber, and the primary RCD clamp.

Key Design Points

- Minimize secondary circuit bias currents. Use low current feedback Zeners for best tolerance. The very low Zener bias current in this design will provide approximately $\pm 10\%$ output voltage tolerance. A precision reference (e.g. TL431) can be used if higher precision is required.
- Design transformer with low reflected voltage to minimize clamp losses. A larger device (TNY266) may allow further reduction in V_{OR} .
- Wind transformer for lowest leakage inductance. Choose wire gauges to completely fill winding layers.
- Winding the transformer with tape between primary layers further reduces intra-winding capacitance and no-load consumption.
- Resistor R7 limits the peak current into the optocoupler LED to prevent damage during unusual transients.

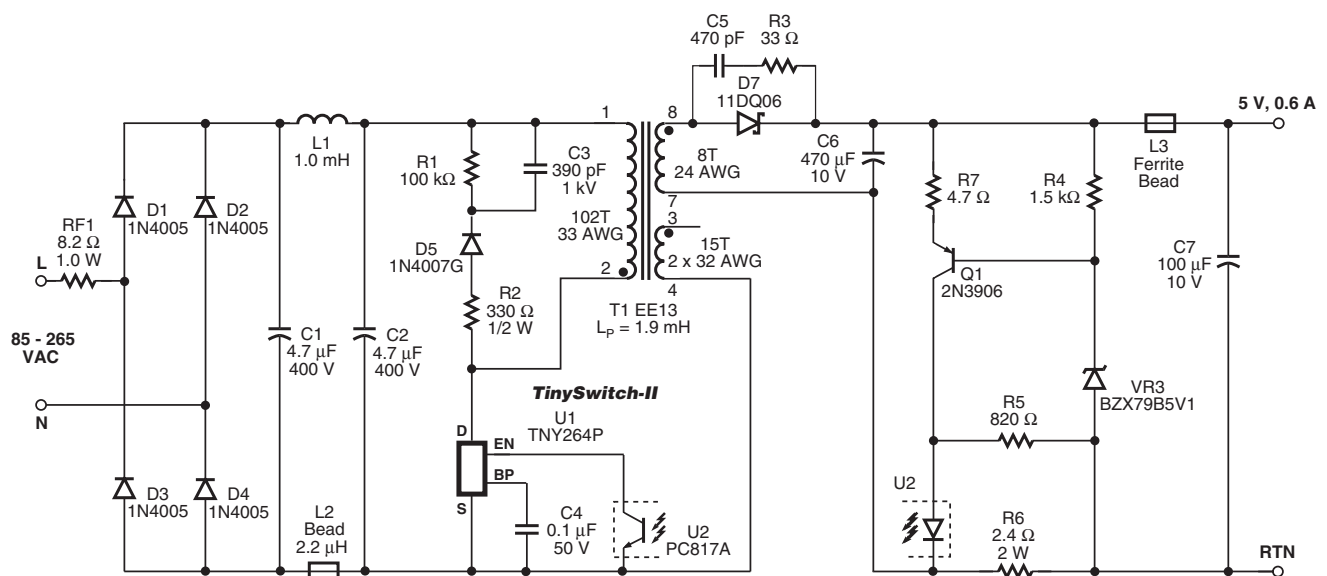


Figure 1. *TinySwitch-II* 3.0 W Cell Phone Charger.

PI-3681-031204

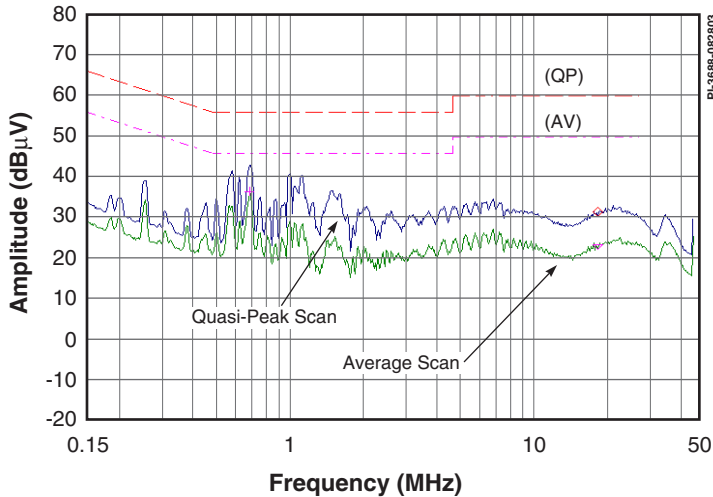


Figure 2. Conducted EMI, Full Load, 230 VAC, Grounded to "Artificial Hand" of LISN.

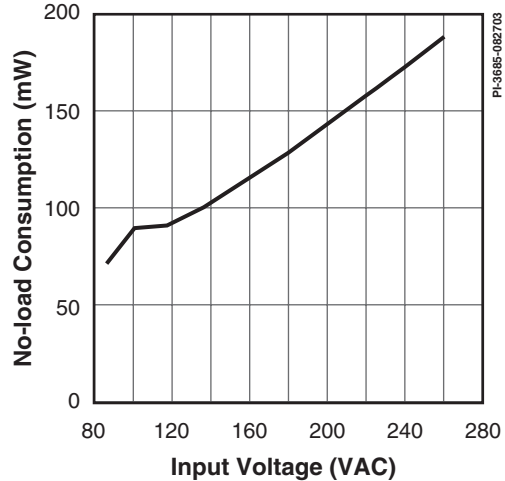


Figure 3. No-load Input Power vs. Line Voltage.

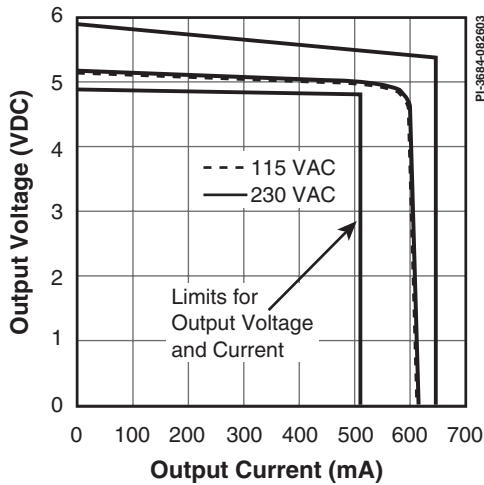


Figure 4. 5.0 VDC, 600 mA CV/CC Curve.

TRANSFORMER PARAMETERS	
Core Material	EE13 TDK PC40, or equivalent A_L of 128 nH/T ²
Bobbin	EE13, 8 pin
Winding Order (pin numbers)	Primary (1-2), tape, Bias (3-4), tape, Secondary (7-8), 5 V, tape
Primary Inductance	1.9 mH \pm 10%
Primary Resonant Frequency	500 kHz (minimum)
Leakage Inductance	50 μ H (maximum)

Table 1. Transformer Construction Information.

For the latest updates, visit www.powerint.com

Power Integrations may make changes to its products at any time. Power Integrations has no liability arising from your use of any information, device or circuit described herein nor does it convey any license under its patent rights or the rights of others. POWER INTEGRATIONS MAKES NO WARRANTIES HEREIN AND SPECIFICALLY DISCLAIMS ALL WARRANTIES INCLUDING, WITHOUT LIMITATION, THE IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF THIRD PARTY RIGHTS. The products and applications illustrated herein (including circuits external to the products and transformer construction) may be covered by one or more U.S. and foreign patents or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at www.powerint.com.

The PI logo, **TOPSwitch**, **TinySwitch**, **LinkSwitch** and **EcoSmart** are registered trademarks of Power Integrations. **PI Expert** and **DPA-Switch** are trademarks of Power Integrations. ©Copyright 2004, Power Integrations

Power Integrations		5245 Hellyer Avenue	San Jose, California 95138
MAIN PHONE NUMBER	APPLICATIONS HOTLINE	APPLICATIONS FAX	For a complete listing of worldwide sales offices, please visit www.powerint.com
+1 408-414-9200	+1 408-414-9660	+1 408-414-9760	

